

# Factoring using $2n+2$ qubits with Toffoli based modular multiplication

Thomas Häner<sup>1,2</sup>   **Martin Roetteler**<sup>2</sup>   Krysta M. Svore<sup>2</sup>

<sup>1</sup>Institute for Theoretical Physics  
ETH Zürich, Switzerland

<sup>2</sup>Quantum Architectures and Computation Group  
Microsoft Research, Redmond, U.S.A.

**[arXiv:1611.07995](https://arxiv.org/abs/1611.07995)**

19th Annual SQInT Workshop  
Baton Rouge, Louisiana  
February 24, 2017

# Outline


- Improved constant increment “+1”
- Toffoli networks for modular multiplication
- Testable circuit for Shor on  $2n+2$  qubits
- Simulations

# How to increment a quantum register?

## Realizing a cyclic shift

How to realize  $x \mapsto x + 1 \pmod{2^n}$ , which cyclically shifts the basis states of an  $n$  qubit register?

### Solution 1: Recursive

 

Good: needs only  $n+1$  qubits  
Bad: needs  $O(n^2)$  gates

### Solution 2: Fourier-style




Good: needs only  $n$  qubits  
Bad: needs  $O(n^2)$  gates  
Ugly: needs rotations

# How to increment a quantum register?

## Realizing a cyclic shift


How to realize  $x \mapsto x + 1 \pmod{2^n}$ , which cyclically shifts the basis states of an  $n$  qubit register?

### Solution 1: Recursive

 

Good: needs only  $n+1$  qubits  
Bad: needs  $O(n^2)$  gates

### Solution 2: Fourier-style

 


Good: needs only  $n$  qubits  
Bad: needs  $O(n^2)$  gates  
Ugly: needs rotations

# How to increment a quantum register?

## Realizing a cyclic shift


How to realize  $x \mapsto x + 1 \pmod{2^n}$ , which cyclically shifts the basis states of an  $n$  qubit register?

### Solution 1: Recursive

 

Good: needs only  $n+1$  qubits  
Bad: needs  $O(n^2)$  gates

### Solution 2: Fourier-style

 


Good: needs only  $n$  qubits  
Bad: needs  $O(n^2)$  gates  
Ugly: needs rotations

# How to increment a quantum register?

## Realizing a cyclic shift


How to realize  $x \mapsto x + 1 \pmod{2^n}$ , which cyclically shifts the basis states of an  $n$  qubit register?

### Solution 1: Recursive

 

Good: needs only  $n+1$  qubits  
Bad: needs  $O(n^2)$  gates

### Solution 2: Fourier-style

 


Good: needs only  $n$  qubits  
Bad: needs  $O(n^2)$  gates  
Ugly: needs rotations

# How to increment a quantum register?

## Realizing a cyclic shift


How to realize  $x \mapsto x + 1 \pmod{2^n}$ , which cyclically shifts the basis states of an  $n$  qubit register?

### Solution 1: Recursive

 

Good: needs only  $n+1$  qubits  
Bad: needs  $O(n^2)$  gates


### Solution 2: Fourier-style

 

Good: needs only  $n$  qubits  
Bad: needs  $O(n^2)$  gates  
Ugly: needs rotations

# How to increment a quantum register?

## Solution 3: Constant folding

 

Good: needs  $O(n)$  gates. Bad: needs  $2n$  qubits


## Solution 4 ???

Is there a circuit with  $n$  qubits, that needs only  $O(n)$  gates?  
Or even just one with  $n + \text{const}$  qubits but  $O(n)$  gates?



# How to increment a quantum register?

## Solution 3: Constant folding

 


Good: needs  $O(n)$  gates. Bad: needs  $2n$  qubits

## Solution 4 ???

Is there a circuit with  $n$  qubits, that needs only  $O(n)$  gates?  
Or even just one with  $n + \text{const}$  qubits but  $O(n)$  gates?

# How to increment a quantum register?

## Solution 3: Constant folding

 

Good: needs  $O(n)$  gates. Bad: needs  $2n$  qubits


## Solution 4 ???

Is there a circuit with  $n$  qubits, that needs only  $O(n)$  gates?

Or even just one with  $n + \text{const}$  qubits but  $O(n)$  gates?

# How to increment a quantum register?

## Solution 3: Constant folding

 


Good: needs  $O(n)$  gates. Bad: needs  $2n$  qubits

## Solution 4 ???


Is there a circuit with  $n$  qubits, that needs only  $O(n)$  gates?  
Or even just one with  $n + \text{const}$  qubits but  $O(n)$  gates?

# Trick from Barenco et al (PRA'95)

 

Note: this uses  $n/2$  “dirty” ancillas qubits.

# Trick from Barenco et al (PRA'95)

 

**Note: this uses  $n/2$  “dirty” ancillas qubits.**



# Incrementer “+1” by Craig Gidney

- Based on the following trick:

$$\begin{aligned} |x\rangle |g\rangle &\mapsto |x - g\rangle |g\rangle \\ &\mapsto |x - g\rangle |g' - 1\rangle \\ &\mapsto |x - g - g' + 1\rangle |g' - 1\rangle \\ &\mapsto |x + 1\rangle |g\rangle \end{aligned}$$

(Note that  $\bar{g} + 1 = g'$ , where  $g'$  denotes two's complement and  $\bar{g}$  denotes one's complement, and that  $g + g' = 0$ ).

- If  $n$  dirty ancillas are available, this allows to implement +1 increment using only  $O(n)$  Toffoli gates.
- If only 1 dirty ancilla is available, precompute final carry, apply a split and recurse. Leads to  $O(n \log n)$  Toffoli gates.

# Incrementer “+1” by Craig Gidney

- Based on the following trick:

$$\begin{aligned} |x\rangle |g\rangle &\mapsto |x - g\rangle |g\rangle \\ &\mapsto |x - g\rangle |g' - 1\rangle \\ &\mapsto |x - g - g' + 1\rangle |g' - 1\rangle \\ &\mapsto |x + 1\rangle |g\rangle \end{aligned}$$

(Note that  $\bar{g} + 1 = g'$ , where  $g'$  denotes two's complement and  $\bar{g}$  denotes one's complement, and that  $g + g' = 0$ ).

- If  $n$  dirty ancillas are available, this allows to implement +1 increment using only  $O(n)$  Toffoli gates.
- If only 1 dirty ancilla is available, precompute final carry, apply a split and recurse. Leads to  $O(n \log n)$  Toffoli gates.

# Incrementer “+1” by Craig Gidney

- Based on the following trick:


$$\begin{aligned} |x\rangle |g\rangle &\mapsto |x - g\rangle |g\rangle \\ &\mapsto |x - g\rangle |g' - 1\rangle \\ &\mapsto |x - g - g' + 1\rangle |g' - 1\rangle \\ &\mapsto |x + 1\rangle |g\rangle \end{aligned}$$

(Note that  $\bar{g} + 1 = g'$ , where  $g'$  denotes two's complement and  $\bar{g}$  denotes one's complement, and that  $g + g' = 0$ ).

- If  $n$  dirty ancillas are available, this allows to implement +1 increment using only  $O(n)$  Toffoli gates.
- If only 1 dirty ancilla is available, precompute final carry, apply a split and recurse. Leads to  $O(n \log n)$  Toffoli gates.



# Carry precomputation w/dirty qubits

 


Works for any constant addition “ $+c$ ” (not just “ $+1$ ”).

Bits are encoded in the presence/absence of orange gates.

This needs  $4(n - 2)$  Toffoli and  $4wt(c)$  Clifford gates.

# Carry precomputation w/dirty qubits

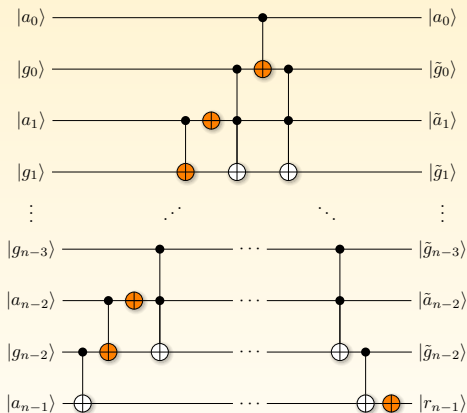


Works for any constant addition “ $+c$ ” (not just “ $+1$ ”).

Bits are encoded in the presence/absence of orange gates.

This needs  $4(n - 2)$  Toffoli and  $4wt(c)$  Clifford gates.

# Carry precomputation w/dirty qubits

 


Works for any constant addition “ $+c$ ” (not just “ $+1$ ”).

Bits are encoded in the presence/absence of orange gates.

This needs  $4(n - 2)$  Toffoli and  $4wt(c)$  Clifford gates.

# Carry precomputation w/dirty qubits

 


Works for any constant addition “ $+c$ ” (not just “ $+1$ ”).


Bits are encoded in the presence/absence of orange gates.

This needs  $4(n - 2)$  Toffoli and  $4wt(c)$  Clifford gates.

# Carry precomputation w/dirty qubits

 

 
## Putting it all together: addition-by-constant




Note that this circuit uses a clean ancilla to detect if the final overflow happened.

However, it is not necessary to use a clean qubit, a dirty qubit suffices as shown next.

# Carry computation using garbage only

 

# Carry computation using garbage only

 

$$T_A(n) = 2T_A\left(\frac{n}{2}\right) + \underbrace{2 \cdot 2\frac{n}{2}}_{\text{incr}} + \underbrace{4\frac{n}{2}}_{\text{carry}}$$


$$= 2T_A\left(\frac{n}{2}\right) + 8n$$

$\vdots$

$$= 8n \log_2 n$$



# Experimental results (addition)

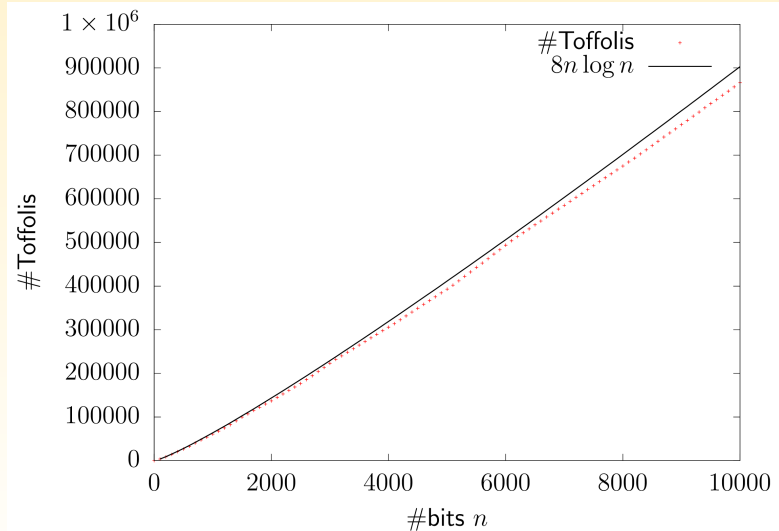

Toffoli circuits implemented and simulated in LIQUi| $\rangle$ .

## Addition-by-constant: comparison

- Fourier-based adder, Draper-style:  
Advantage: Ancilla-free  
Disadvantage:  $\Theta(n^2)$  gates, not exact
- Cuccaro et al adder, with folded constants:  
Advantage:  $O(n)$  runtime  
Disadvantage: Requires  $n + 1$  extra (clean) qubits
- Takahashi et al adder, with folded constants:  
Advantage:  $O(n)$  runtime  
Disadvantage: Requires  $n$  extra (clean) qubits

## Addition-by-constant: comparison

- Fourier-based adder, Draper-style:  
Advantage: Ancilla-free  
Disadvantage:  $\Theta(n^2)$  gates, not exact
- Cuccaro et al adder, with folded constants:  
Advantage:  $O(n)$  runtime  
Disadvantage: Requires  $n + 1$  extra (clean) qubits
- Takahashi et al adder, with folded constants:  
Advantage:  $O(n)$  runtime  
Disadvantage: Requires  $n$  extra (clean) qubits
- **Our adder:**  
Advantage: Toffoli-based, only 1 extra (dirty) qubit  
Disadvantage:  $\Theta(n \log n)$  runtime

# Application: modular exponentiation

## Shor's algorithm

Finds period  $r$  of  $f(x) = a^x \bmod N$ , where  $a, N$  constant.

$$\begin{aligned} a^x \bmod N &= a^{x_m \cdot 2^m} \dots a^{x_1 \cdot 2^1} \cdot a^{x_0 \cdot 2^0} \bmod N \\ &= (a^{2^m} \bmod N)^{x_m} \dots (a^{2^1} \bmod N)^{x_1} \cdot (a^{2^0} \bmod N)^{x_0} \end{aligned}$$

# Application: modular exponentiation

## Shor's algorithm

Finds period  $r$  of  $f(x) = a^x \bmod N$ , where  $a, N$  constant.

$$\begin{aligned} a^x \bmod N &= a^{x_m \cdot 2^m} \dots a^{x_1 \cdot 2^1} \cdot a^{x_0 \cdot 2^0} \bmod N \\ &= (a^{2^m} \bmod N)^{x_m} \dots (a^{2^1} \bmod N)^{x_1} \cdot (a^{2^0} \bmod N)^{x_0} \end{aligned}$$

- Start with  $|y = 1\rangle |x_0\rangle$
- For  $i = 0, \dots, m$ , apply the operator


$$\sum_y \left| (a^{2^i} y) \bmod N \right\rangle \langle y | \otimes |1\rangle \langle 1| + \mathbb{1} \otimes |0\rangle \langle 0|$$

to  $|y\rangle |x_i\rangle$ .

- Final state:

$$|a^x \bmod N\rangle |x\rangle$$

# Shor's algorithm, PE style

 

Note that computing a modular multiplication


$$\begin{aligned} ax \bmod N &= a \cdot (2^m x_m + \dots + 2x_1 + x_0) \bmod N \\ &= ((2^m a) \bmod N)x_m \oplus \dots \oplus ((2a) \bmod N)x_1 \oplus ax_0 \end{aligned}$$

can be done using  $m + 1$  controlled modular additions

Controlled multiplication  $\Rightarrow$  Doubly-controlled modular additions

How to perform modular additions?

# Shor's algorithm, PE style

 

Note that computing a modular multiplication


$$\begin{aligned} ax \bmod N &= a \cdot (2^m x_m + \dots + 2x_1 + x_0) \bmod N \\ &= ((2^m a) \bmod N)x_m \oplus \dots \oplus ((2a) \bmod N)x_1 \oplus ax_0 \end{aligned}$$

can be done using  $m + 1$  controlled modular additions

Controlled multiplication  $\Rightarrow$  Doubly-controlled modular additions

How to perform modular additions?

# Shor's algorithm, PE style

 

Note that computing a modular multiplication

$$\begin{aligned} ax \bmod N &= a \cdot (2^m x_m + \dots + 2x_1 + x_0) \bmod N \\ &= ((2^m a) \bmod N)x_m \oplus \dots \oplus ((2a) \bmod N)x_1 \oplus ax_0 \end{aligned}$$


can be done using  $m + 1$  controlled modular additions

Controlled multiplication  $\Rightarrow$  Doubly-controlled modular additions

How to perform modular additions?



 
## Modular addition: requires 3 integer additions



Ultimately, the  $b$  register holds the value  $r = a + b \bmod N$ , where  $a$  is the constant to be added.

This method was used in van Meter and Itoh [4] and Takahashi and Kunihiro [5].
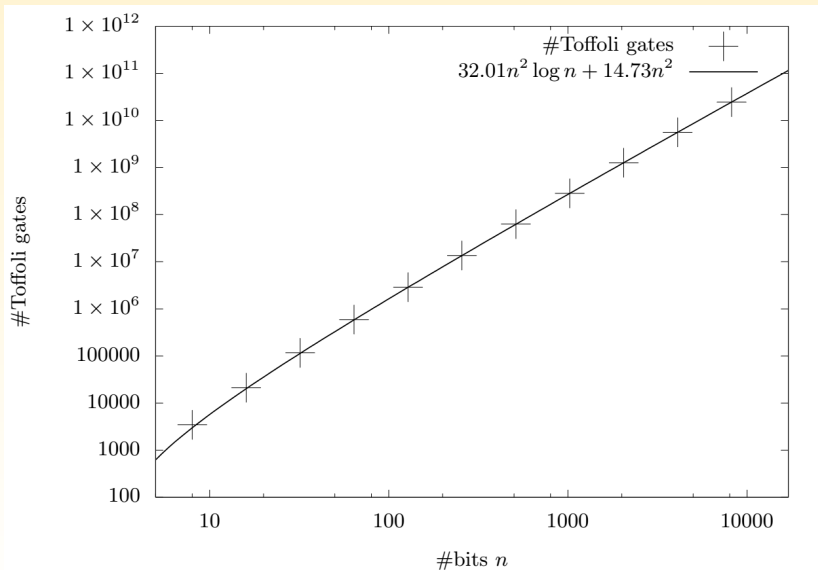
# Scaling results (modular multiplication)



# Resource estimates for Shor's algorithm

	Takahashi et al	Our implementation
Runtime (exact)	$\Theta(n^4 \log \frac{1}{\epsilon})$	$\Theta(n^3 \log n)$
Runtime (approx.)	$\Theta(n^3 \log \frac{n}{\epsilon} \log \frac{1}{\epsilon})$	n/a
Depth	$\Theta(n^3 \log \frac{1}{\epsilon})$	$\Theta(n^3)$
Space	$2n + 2$	$2n + 2$


**Bonus feature:** Our modular multiplication circuit can be tested and debugged efficiently!

## Resource estimates for Shor's algorithm

	Takahashi et al	Our implementation
Runtime (exact)	$\Theta(n^4 \log \frac{1}{\epsilon})$	$\Theta(n^3 \log n)$
Runtime (approx.)	$\Theta(n^3 \log \frac{n}{\epsilon} \log \frac{1}{\epsilon})$	n/a
Depth	$\Theta(n^3 \log \frac{1}{\epsilon})$	$\Theta(n^3)$
Space	$2n + 2$	$2n + 2$


**Bonus feature:** Our modular multiplication circuit can be tested and debugged efficiently!

# Toffoli networks: debugging

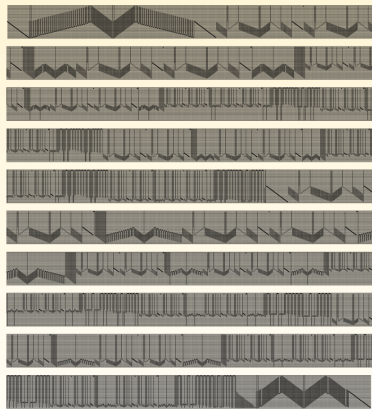


Toffoli network to implement modular addition of the constant value 65,521 to a 16-qubit register.

# Toffoli networks: debugging

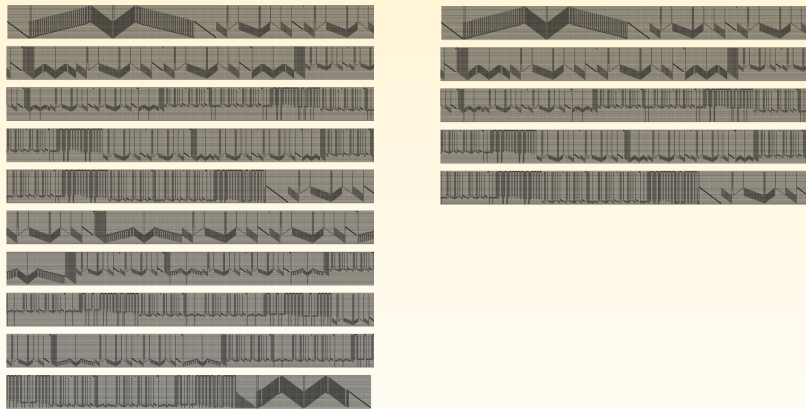


Toffoli network to implement modular addition of the constant value 65,521 to a 16-qubit register. Partial executions.

# Toffoli networks: debugging

 

Toffoli network to implement modular addition of the constant value 65,521 to a 16-qubit register. Partial executions.

 
# Hierarchical debugging of Toffoli circuits



**Remark:** If chosen test vectors trigger all faults that might be present in the circuit, this method allows to localize all faults.


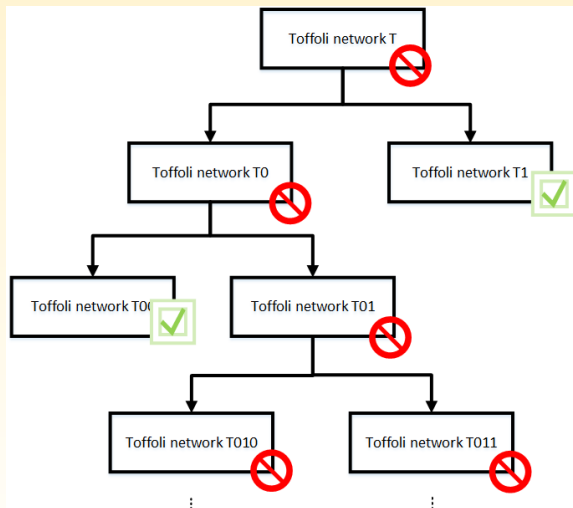
# Hierarchical debugging of Toffoli circuits



**Remark:** If chosen test vectors trigger all faults that might be present in the circuit, this method allows to localize all faults.

# References



Thomas G Draper.

Addition on a quantum computer.

*arXiv preprint quant-ph/0008033*, 2000.



Yasuhiro Takahashi, Seiichiro Tani, and Noboru Kunihiro.

Quantum addition circuits and unbounded fan-out.

*arXiv preprint arXiv:0910.2530*, 2009.



Craig Gidney.

Creating bigger controlled nots from Toffoli gates, without workspace.

<http://cs.stackexchange.com/questions/40933/>, 2015.



Rodney van Meter and Kohei M. Itoh.

Fast quantum modular exponentiation.

*Physical Review A*, 71:052320, 2005.



Yasuhiro Takahashi and Noboru Kunihiro.

A quantum circuit for Shor's factoring algorithm using  $2n + 2$  qubits.

*Quantum Information & Computation*, 6(2):184–192, 2006.